

Third Semester B.E. Degree Examination, December 2015
Information Science and Engineering
Principles of analog and Digital Design (14IS32)

Time: 3Hrs

Max. Marks: 100

- Instructions:** 1. Answer one full question from each unit.
 2. Any missing Data can be suitably assumed.

UNIT-I

- | | Marks | Course Outcome, Blooms Level |
|---|----------|------------------------------|
| 1. a. Draw the transconductance curve and drain curves for E-MOSFET. How inversion layer in E-MOSFET helps in conduction? Explain | 10 Marks | CO2, L2 |
| b. Given $V_{gs(off)} = -2V$, $I_{dss} = 6mA$. Find the values of I_{ds} for the following values of V_{gs} of D-MOSFET | 06 Marks | CO1, CO2, L3 |
| a) $V_{gs} = -4V$ | | |
| b) $V_{gs} = -6V$ | | |
| c) $V_{gs} = +3V$ | | |
| c. What is active load switching? Explain | 04 Marks | CO1, L1 |
| 2. a. With necessary circuit diagram, drain curves and trans conductance curves, brief the operation of D-MOSFET | 10 Marks | CO2, L3 |
| b. What is passive load switching? Explain with necessary diagram. | 05 Marks | CO1, L2 |
| c. Write a short note on CMOS and its applications. | 05 Marks | CO1, L1 |

UNIT-II

- | | | |
|--|----------|--------------|
| 3. a. What is universal gate? Implement the basic gates using universal gates. | 05 Marks | CO1, L3 |
| b. Minimize the expressions, using K-map
$Y = A\bar{B}C + \bar{A}BC + \bar{A}B\bar{C} + A\bar{B}\bar{C}$
$Y = \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D + A\bar{B}C\bar{D} + A\bar{B}CD$ | 08 Marks | CO2, L5 |
| c. Explain parity generator and checker in detail | 07 Marks | CO2, L4 |
| 4. a. Simplify the expression using boolean laws and theory
i. $X = (\bar{A} + B)(A + B + C)\bar{D}$
ii. $Z = (\bar{A} + B)(A + \bar{B})$ | 05 Marks | CO1, CO2, L5 |
| b. Using graphical procedure, obtain a NOR-gate realization of the boolean expression.
$f(a, b, c, d) = \bar{a}d + a\bar{d}(b + \bar{c})$ | 05 Marks | CO2, L5 |
| c. What is K-map? Explain in detail how to simplify the expression using K-map by grouping the minterms. Also simplify
$f(x, y, z) = \sum m(0, 1, 4) + \sum dc(3, 7)$ | 10 Marks | CO1, L5 |


UNIT-III

- | | | |
|---|----------|---------|
| 5. a. List and Explain the different types of Flip-Flops with truth table and excitation table. | 09 Marks | CO3, L1 |
| b. Explain the working of NAND gate latch circuit. | 06 Marks | CO3, L1 |
| c. Discuss the effect of propagation delay in a Flip-Flop circuit. | 05 Marks | CO3, L2 |
| 6. a. Explain any two application of Flip-Flops in detail.
Briefly discuss the working of JK master-Slave Flip Flop. | 10 Marks | CO3, L2 |
| b. | 05 Marks | CO3, L2 |
| c. What is switch contact Bounce problem? How it is overcome by S-R Flip-Flop? Explain. | 05 Marks | CO3, L3 |

UNIT-IV

- | | | |
|--|----------|---------|
| 7. a. Differentiate between synchronous counters and Asynchronous counter. | 05 Marks | CO3, L3 |
|--|----------|---------|

 - b. Explain four bit ripple counter along with the circuit diagram and waveform
 - c. What is presentable counters? Explain
8.
 - a. Explain the advantages of synchronous counter over Asynchronous counter.
 - b. Design the following state transition diagram using JKFF



Show the design and circuit diagram

- c. Explain 3-bit binary Asynchronous up-down counter, along with the waveforms

UNIT-V

9. a. Find out voltages caused by the following
 a) Each bit in a 5 bit ladder
 b) Output voltage for digital input 10111
 Assume $0=0V$ and $1 = +10V$
 b. Illustrate the working of R-ZR ladder for the digital input 0010
 c. Discuss the process of successive approximation.
10. a. Differentiate between Resistive divider method and R-ZR method.
 b. Write a neat diagram explain the conversion of analog to digital using counter method.
 c. Throw light on the different testing methods involved in a simple DAC machine.